

FULL SUBTRACTOR:


The full subtractor consists of three inputs and two outputs. Let, the three inputs denotes the minuend, subtrahend and previous borrow as A , B , B_{in} . The output are D and B_{out} represents difference and Borrow.

The full subtractor is a combinational circuit that performs the subtraction operation.

These subtractors are used in processors to compute tables, addresses, etc..

Truth table:—

A	B	B_{in}	D	B_{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	0	1	1

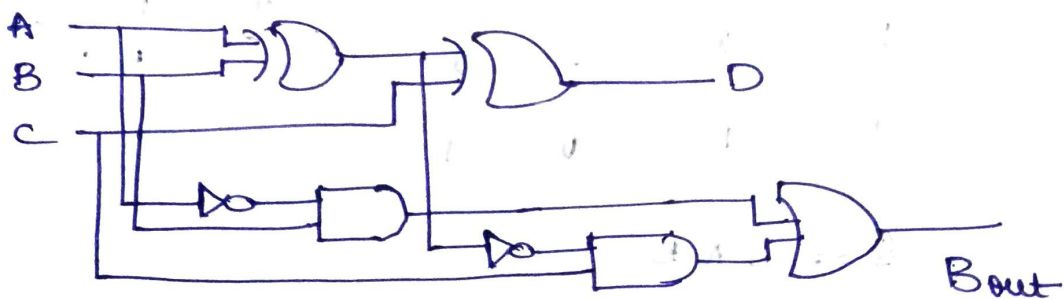

$$D = A \oplus B \oplus B_{in}$$

$$B_{out} = (A \oplus B) \cdot C + (A \oplus B) \cdot (B \oplus C)$$